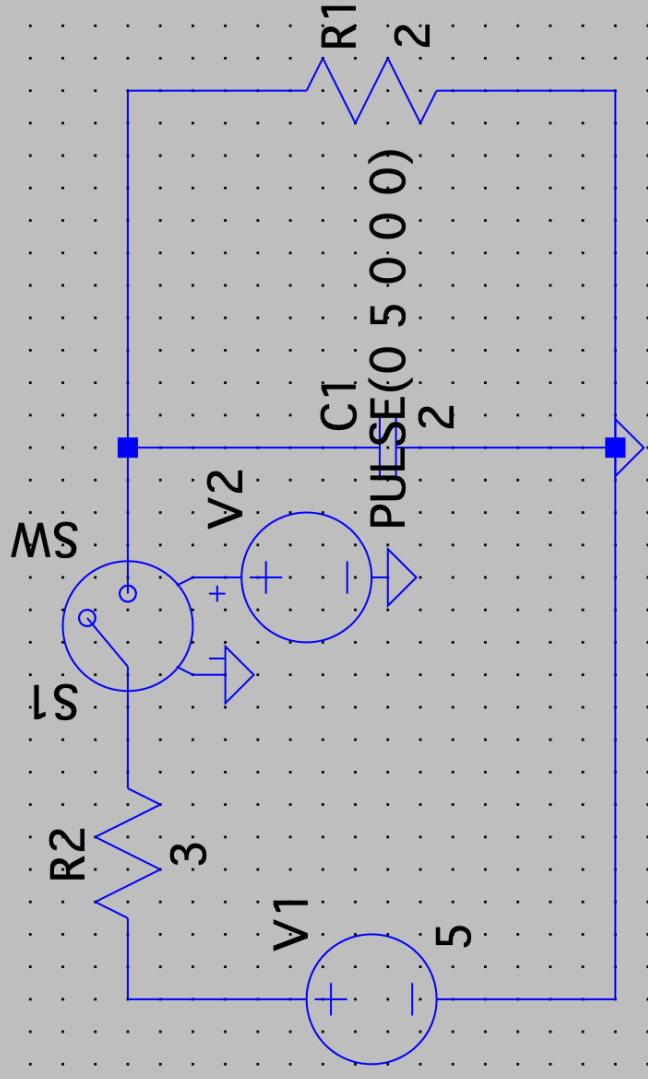


Calculate initial voltage and steady state voltage across the capacitor.
 Plot voltage across capacitor and current through capacitor for $t > 0$ sec.



.tran 10

.model SW SW()

