

Refer to the RL circuit in fig. If 10 V is applied to the input,  
Find the magnitude and the phase shift produced at 5 khz.  
Specify wheather the phase shift is leading or lagging.

