


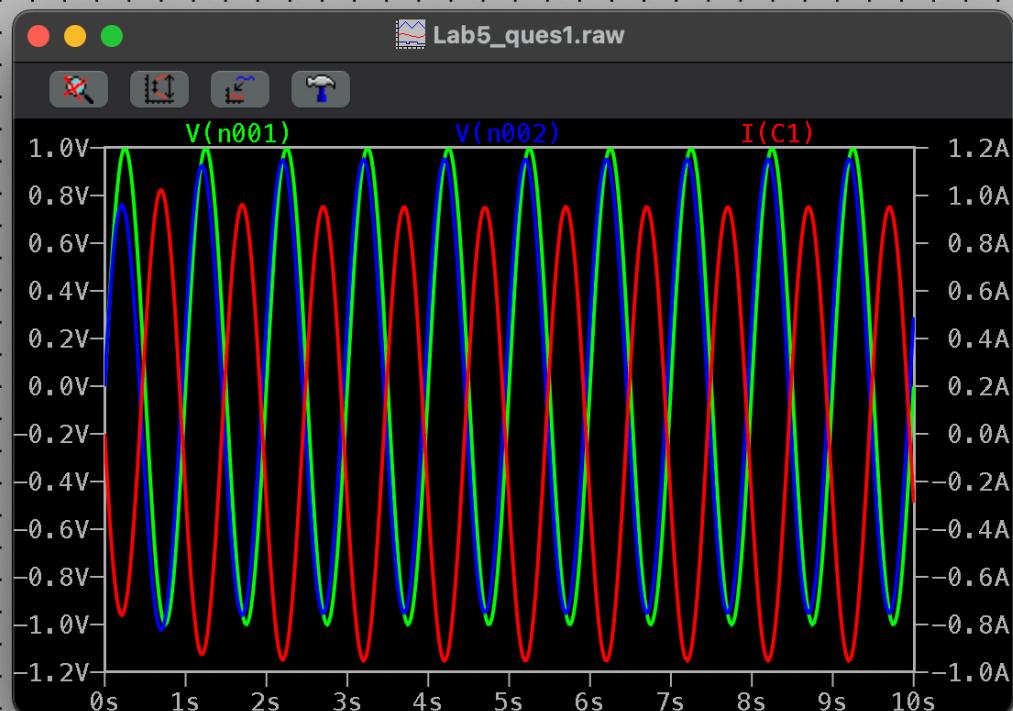


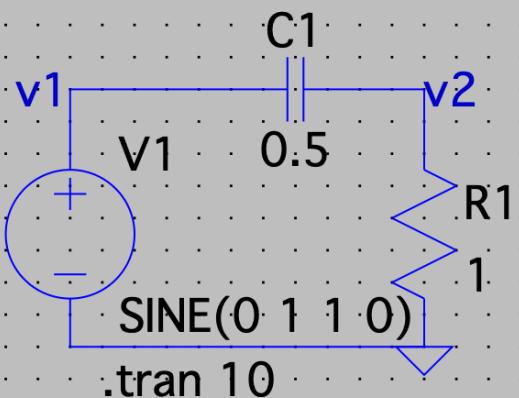
Transient Analysis of AC Circuits First order
(order is number of elements that are energy absorber)



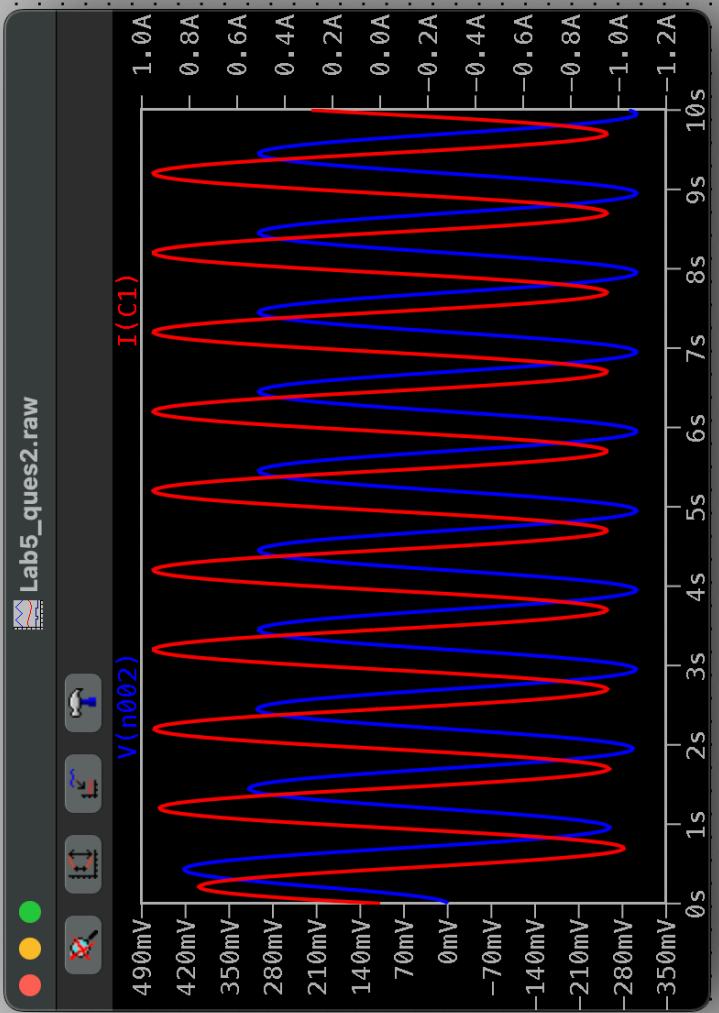



calculate $V_0(t)$ for $t > 0$

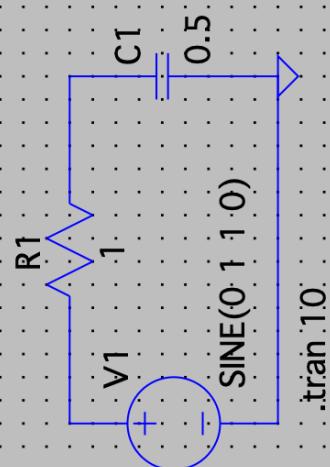

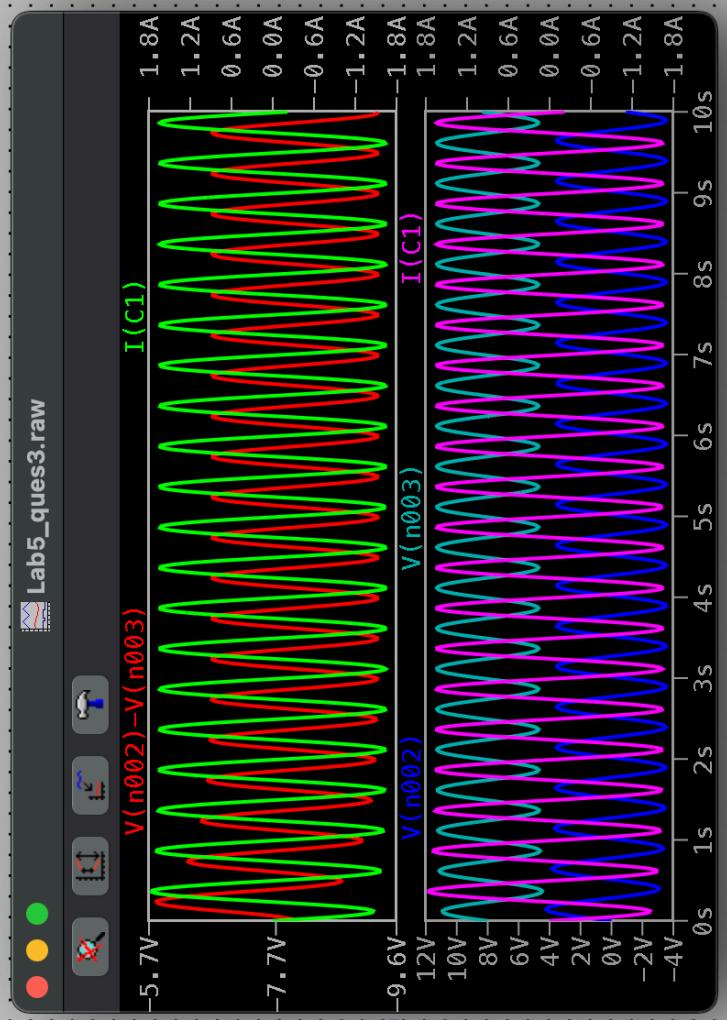


calculate $v_{C1}(t)$ for $t > 0$


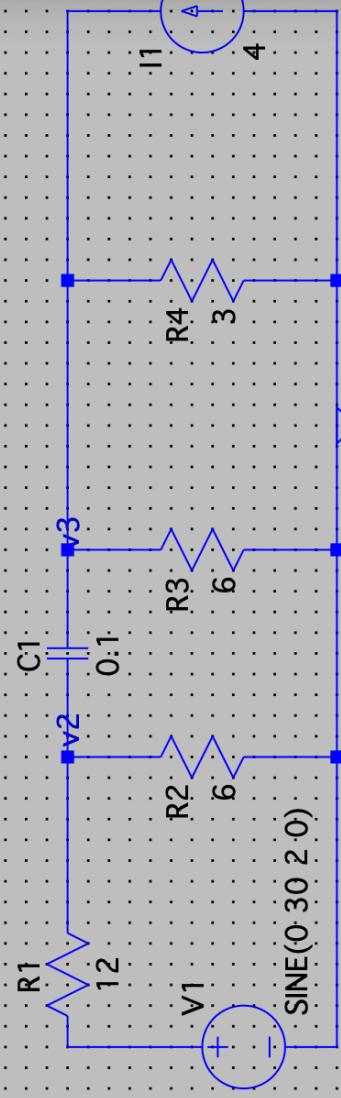


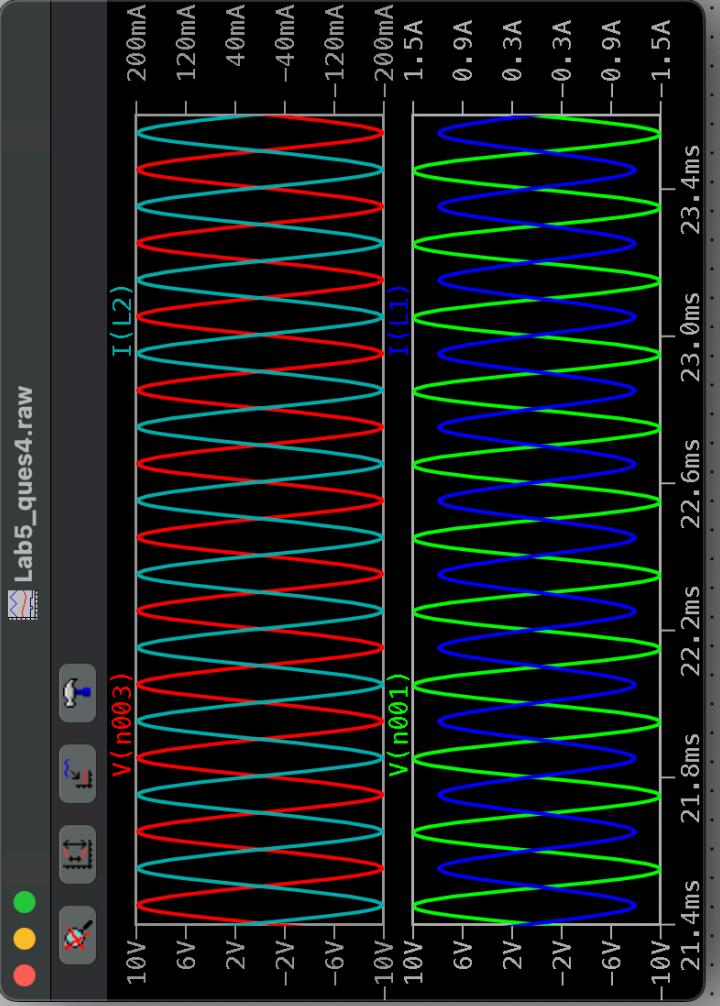


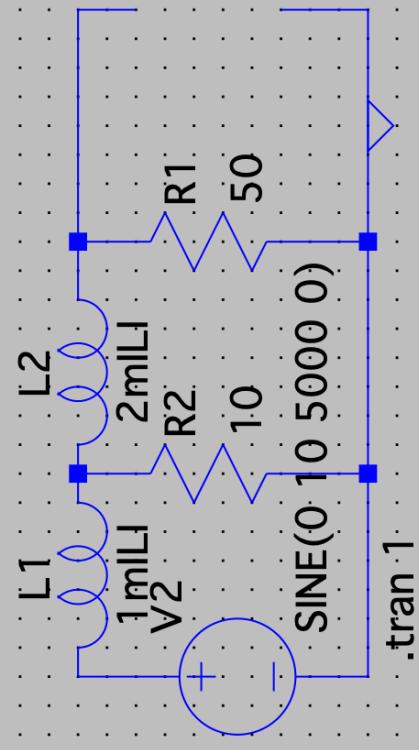Refer to the RL circuit in fig. If 10 V is applied to the input, Find the magnitude and the phase shift produced at 5 khz. Specify whether the phase shift is leading or lagging.



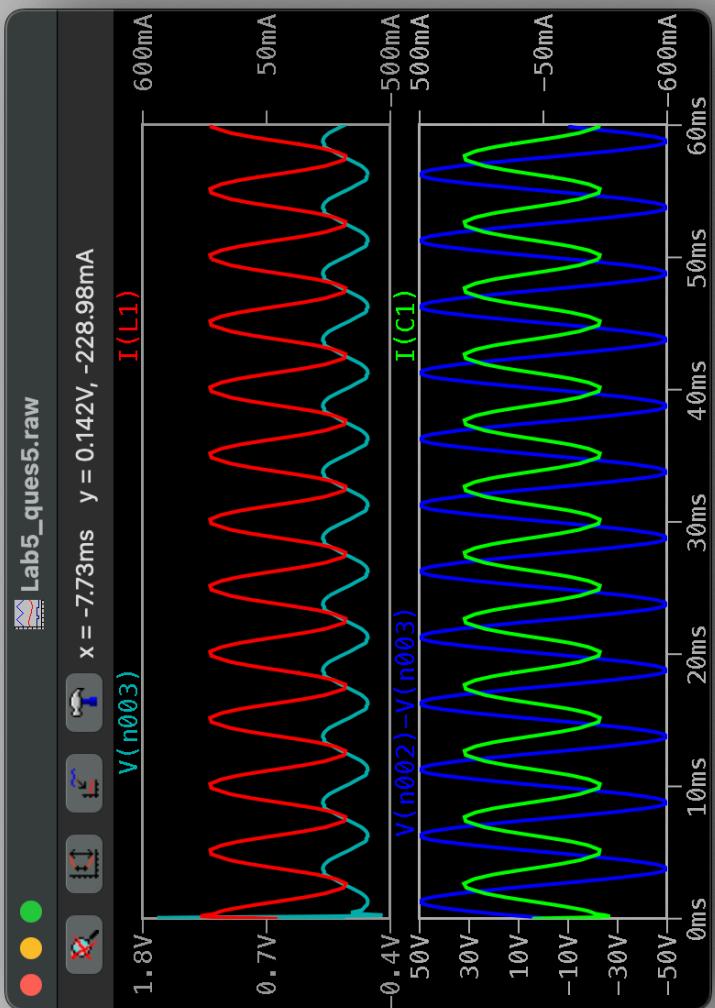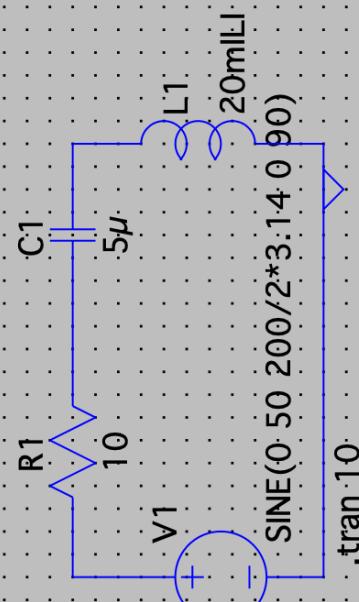Find current i in the circuit of Fig. when $v_s(t) = 50 \cos 200t \text{ V}$.



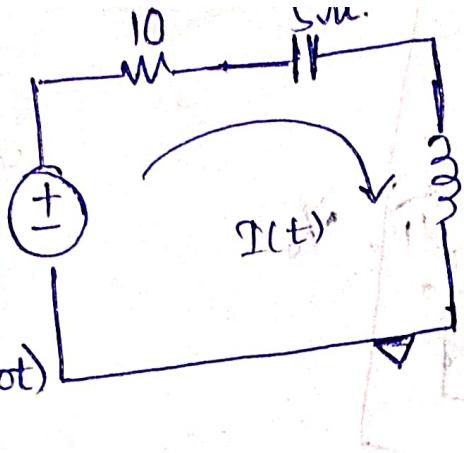

$$V(t) \Rightarrow \\ 50 \sin \\ (90 + 200t)$$

20mH

$\frac{1}{j\omega C}$

$(R + j\omega L)$

$$V(t) \Rightarrow 10I(t) + 5\pi \cdot I(t) + j\omega L \cdot I(t)$$

$$V(t) \Rightarrow (10I(t)) \left[10 + \frac{1}{j\omega C} + j\omega L \right]$$

$$Z \Rightarrow R + \frac{1}{j\omega C} + j\omega L$$

$$\therefore Z \Rightarrow \sqrt{R^2 + \left[\frac{1}{\omega^2 C^2} + \omega^2 L^2 \right]}$$

$$= \sqrt{0.0001 + 0.000004 + 0.00000004} = \sqrt{0.0001000004} = 0.01000002$$

$$= \frac{V(t)}{10 + \frac{1}{j\omega C} + j\omega L}$$


$\tan^{-1} \left[\frac{L}{R} \right]$

- 89°

$$= \frac{50 \sin(90 + 200t)}{\sqrt{10^2 + \left[\frac{1}{\omega^2 C^2} + \omega^2 L^2 \right]}} e^{j\theta} \quad \theta = \tan^{-1} \left[\frac{1}{10} \right]$$

$$= 0.0667 e^{j89}$$

4)

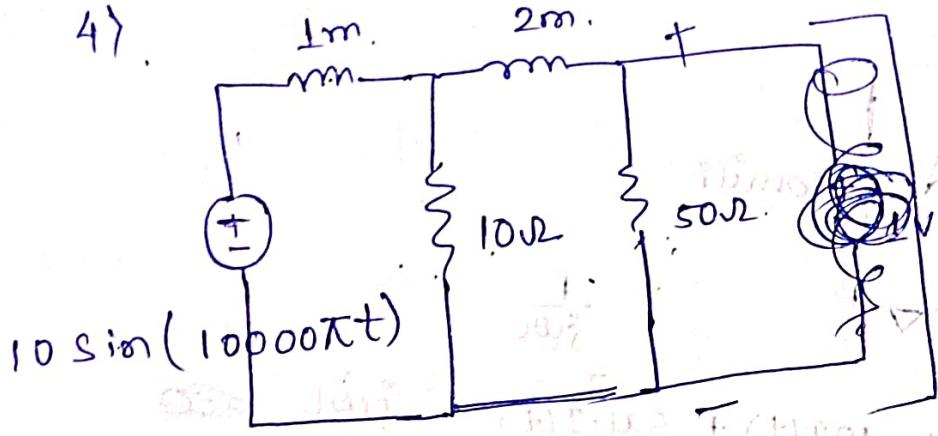

$$\omega t = f = \frac{1}{2\pi L}$$

$$2\pi f = \omega$$

~~$$\omega = 10000$$~~

~~$$\omega = 10000$$~~

$$\Rightarrow ((j \cdot 2 \times 10^{-3} \cdot \omega) + 50) // 10 \text{ series } (1 \times 10^3 \cdot \omega \cdot j)$$

$$\Rightarrow (20^\circ + 50^\circ) // 10 \text{ series } (10^\circ)$$

$$\frac{200^\circ + 50^\circ}{20^\circ + 60} + 10^\circ$$

$$\Rightarrow \frac{(400^\circ + 1100^\circ)}{20^\circ + 60} = \frac{200^\circ + 500 + 200^\circ + 600^\circ}{20^\circ + 60}$$

$$= \frac{800^\circ + 300^\circ}{20^\circ + 60} \times \frac{20^\circ + 60}{10^\circ}$$

$$\Rightarrow \frac{\sqrt{74}(8^\circ + 3^\circ)}{1^\circ + 9^\circ} \Rightarrow$$

$$\frac{V}{Z} = I$$

$$I = \frac{10 \angle 60^\circ}{\sqrt{74}(13.51 \angle 51.01)}$$

(1)

$$\sqrt{74} \rightarrow \frac{80^\circ + 36^\circ}{2^\circ + 6^\circ}$$


$$= \frac{40^\circ + 15^\circ}{1^\circ + 3^\circ} \angle 69.44^\circ$$

$$= \sqrt{(40)^2 + (15)^2 - 1600 + 225} \approx 1182 \approx 42.72$$

$$= \sqrt{10^2 - \frac{42.72^2}{13.51}}$$

$$= -13.51 \angle 51.01^\circ$$

2). Calc^u $V_o(t)$ for $t > 0$.

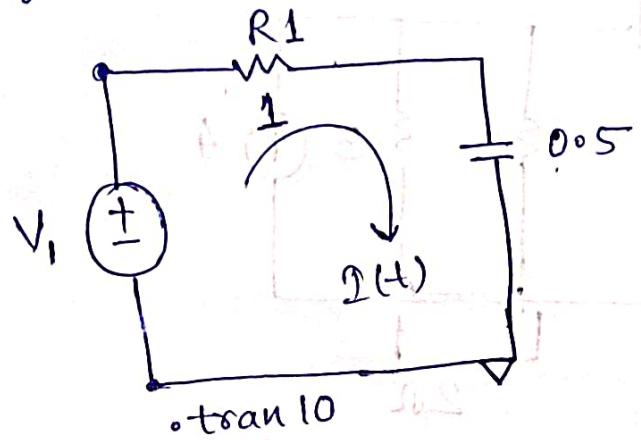


$$V(t) = I \sin(\omega t) \Rightarrow I(t) \cdot R + I(t) \cdot \frac{1}{j\omega C} = 0.5$$

$$V(t) \Rightarrow I(t) \left[1 + \frac{2}{j\omega C} \right] = 0.5 \quad \text{or} \quad [1 - 2j]$$

$$V(t) \Rightarrow I(t) \left[1 + \frac{2}{j} \right] = 0.5 \quad \text{or} \quad \frac{\sin(t)}{\sqrt{1^2 + (\frac{2}{j})^2}} \angle 20^\circ$$

$$I(t) \Rightarrow \frac{V(t)}{Z_{im}} = \frac{\frac{1}{j} \sin(t) \angle 20^\circ}{\sqrt{1^2 + (\frac{2}{j})^2}} \Rightarrow \frac{\sin(t) \angle 20^\circ}{\sqrt{5} \angle -63.43^\circ} = 0.4472 \angle 63.43^\circ$$

1)




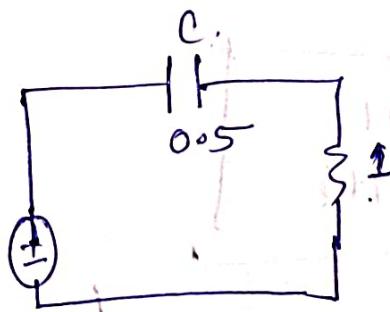


\Rightarrow Same ans as (2).

$$R \left[\frac{0.5}{j\omega C} + j \right] \angle 0^\circ = 0$$

$$\left[\frac{0.5}{j\omega C} + j \right] \angle 0^\circ = 0$$

3).

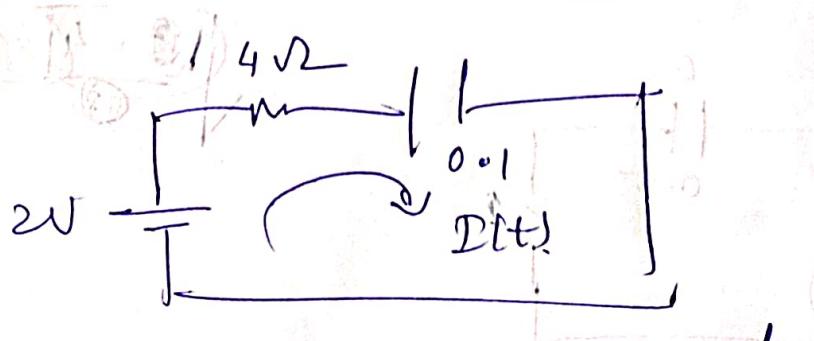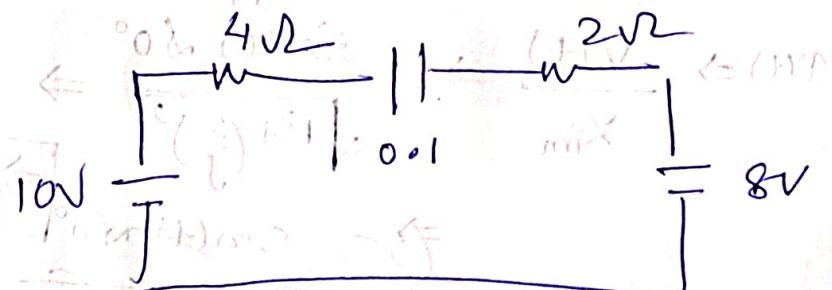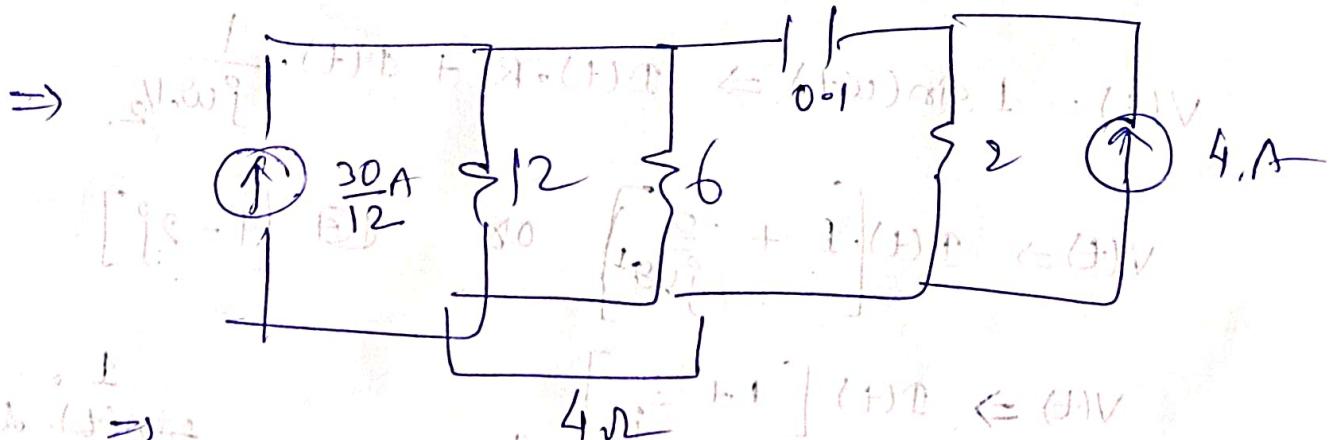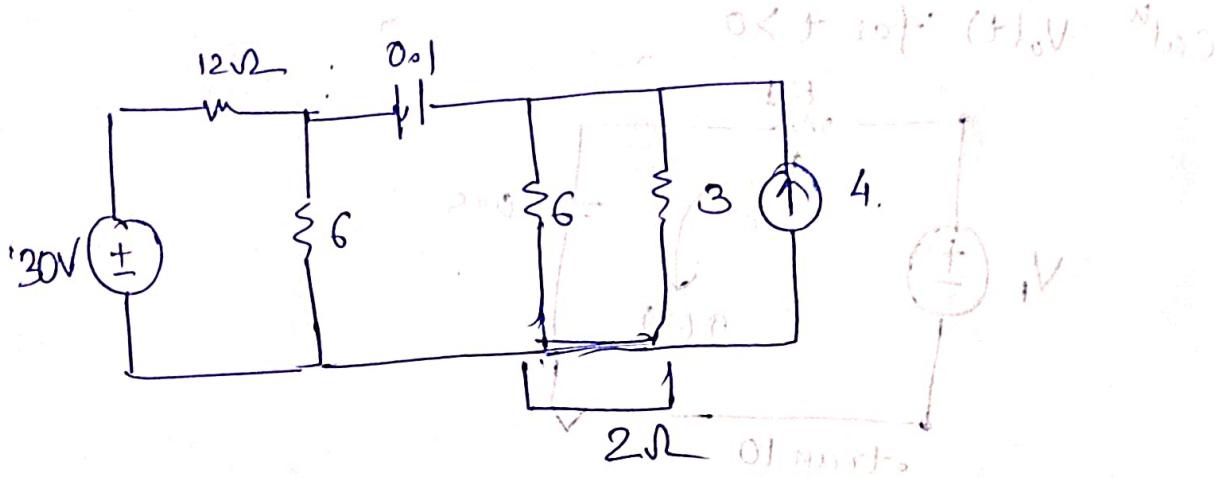

$$\Rightarrow 2 = I(t) \cdot 4 + \frac{1}{0.01} \omega_0^2 \cdot I(t)$$

$$2 = I(t) \left[4 + \frac{10}{\omega_0^2} \right] \text{ A}$$

$$\Rightarrow 2 = I(t) [4 - 2.5\pi^2]$$

$$\theta = \tan^{-1} \left[\frac{b}{a} \right]$$

$$\theta \Rightarrow \tan^{-1} \left[\frac{2.5}{4} \right]$$

$$\Rightarrow D(t) \Rightarrow \frac{2 \angle 0^\circ}{\sqrt{4^2 + (2.5)^2}} \propto -32.005 \text{ degree.}$$

$$\Rightarrow \frac{2}{4.071} \angle 0^\circ \propto -32.005$$

$$\Rightarrow \boxed{\begin{array}{l} 0.42 \propto 32.005 \\ \sqrt{0.42} \end{array}}$$