



.op

.step param R 1 21 2

Determine the maximum power that can be delivered to the variable resistor R in the circuit.

