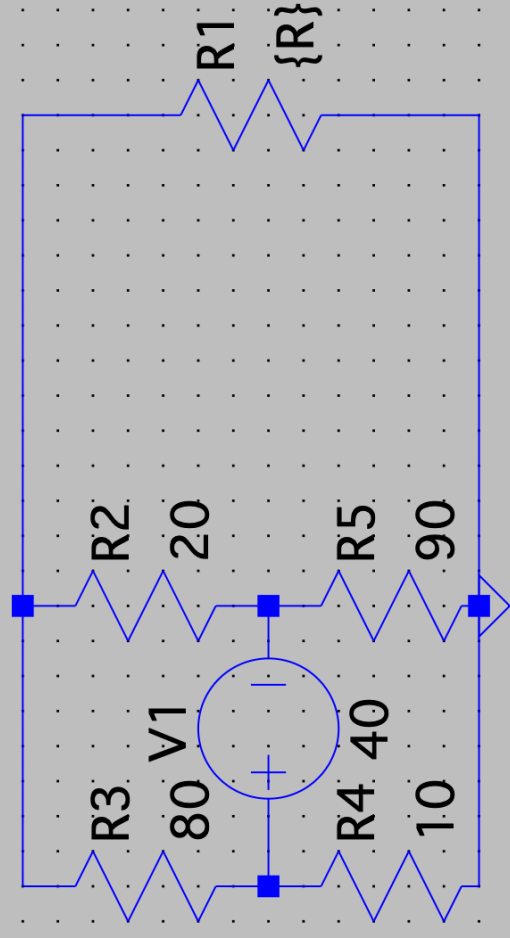


Calculate the value of R for maximum power, and also determine the maximum power absorbed by R



.op

.step param R 1 100 5

