

In the network shown below, the switch is closed to position 1 at $t=0$ & is moved to position 2 at $t = 0.4$. Determine the voltage across the capacitor $V_c(t)$ & sketch it for $0 \leq t \leq 1$ sec. Also find the value of 't' for which $V_c(t) = 0$

