

Find current i in the circuit of Fig. when $v_s(t) = 50 \cos 200t$ V.

