

In the circuit shown, the switch is closed at  $t = 0$  sec. so, calculate voltage across the capacitor for  $t > 0$ .

